

# A new connection between irreversible random walks and electric networks

Work in progress, joint with  
Áron Folly

Márton Balázs

University of Bristol

Combinatorics and Statistical Mechanics  
Warwick, April 2014.

## Reversible chains and resistors

- Reducing a network

- Thomson, Dirichlet principles

- Monotonicity, transience, recurrence

## Irreversible chains and electric networks

- The part

- From network to chain

- From chain to network

- Effective resistance

- What works

## The electric network

- Reducing the network

- Nonmonotonicity

- Dirichlet principle


## Reversible chains and resistors

**Irreducible Markov chain:** on  $\Omega$ ,  $a \neq b$ ,  $x \in \Omega$ ,

$$h_x := \mathbf{P}_x\{\tau_a < \tau_b\} \quad (\tau \text{ is the hitting time})$$

is **harmonic**:
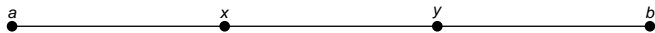
$$h_x = \sum_y P_{xy} h_y, \quad h_a = 1, \quad h_b = 0.$$




## Reversible chains and resistors

**Irreducible Markov chain:** on  $\Omega$ ,  $a \neq b$ ,  $x \in \Omega$ ,

$$h_x := \mathbf{P}_x\{\tau_a < \tau_b\} \quad (\tau \text{ is the hitting time})$$

is **harmonic**:
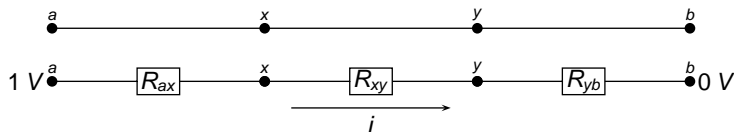
$$h_x = \sum_y P_{xy} h_y, \quad h_a = 1, \quad h_b = 0.$$



**Electric resistor network:** the voltage  $u$  is **harmonic** ( $C = 1/R$ ):

$$u_x = \sum_y \frac{C_{xy}}{\sum_z C_{xz}} \cdot u_y; \quad u_a = 1, \quad u_b = 0.$$


## Reversible chains and resistors

**Irreducible Markov chain:** on  $\Omega$ ,  $a \neq b$ ,  $x \in \Omega$ ,

$$h_x := \mathbf{P}_x\{\tau_a < \tau_b\} \quad (\tau \text{ is the hitting time})$$

is **harmonic**:
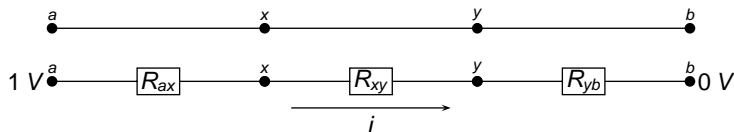
$$h_x = \sum_y P_{xy} h_y, \quad h_a = 1, \quad h_b = 0.$$



**Electric resistor network:** the voltage  $u$  is **harmonic** ( $C = 1/R$ ):

$$u_x = \sum_y \frac{C_{xy}}{\sum_z C_{xz}} \cdot u_y; \quad u_a = 1, \quad u_b = 0.$$

## Reversible chains and resistors

Thus,

$$P_{xy} = \frac{C_{xy}}{\sum_z C_{xz}}$$

## Reversible chains and resistors

Thus,

$$P_{xy} = \frac{C_{xy}}{\sum_z C_{xz}} =: \frac{C_{xy}}{C_x}.$$

---

$$P_{xy} = C_{xy}/C_x$$

## Reversible chains and resistors

Thus,

$$P_{xy} = \frac{C_{xy}}{\sum_z C_{xz}} =: \frac{C_{xy}}{C_x}.$$

Stationary distribtuion:

$$\mu_x = \sum_y \mu_y P_{yx} = \sum_y \mu_y \frac{C_{xy}}{C_y}$$

$$C_x = \sum_y C_y \frac{C_{xy}}{C_y}$$

---

$$P_{xy} = C_{xy}/C_x$$



## Reversible chains and resistors

Thus,

$$P_{xy} = \frac{C_{xy}}{\sum_z C_{xz}} =: \frac{C_{xy}}{C_x}.$$

Stationary distribtuion:

$$\mu_x = \sum_y \mu_y P_{yx} = \sum_y \mu_y \frac{C_{xy}}{C_y}$$

$$C_x = \sum_y C_y \frac{C_{xy}}{C_y}$$

$$\rightsquigarrow C_x = \mu_x.$$

---

$$P_{xy} = C_{xy}/C_x$$

## Reversible chains and resistors

Thus,

$$P_{xy} = \frac{C_{xy}}{\sum_z C_{xz}} =: \frac{C_{xy}}{C_x}.$$

Stationary distribution:

$$\mu_x = \sum_y \mu_y P_{yx} = \sum_y \mu_y \frac{C_{xy}}{C_y}$$

$$C_x = \sum_y C_y \frac{C_{xy}}{C_y}$$

$$\rightsquigarrow C_x = \mu_x.$$

---

$$P_{xy} = C_{xy}/C_x$$

$$C_x = \mu_x$$

## Reversible chains and resistors

Thus,

$$P_{xy} = \frac{C_{xy}}{\sum_z C_{xz}} =: \frac{C_{xy}}{C_x}.$$

Stationary distribtuion:

$$\mu_x = \sum_y \mu_y P_{yx} = \sum_y \mu_y \frac{C_{xy}}{C_y}$$

$$C_x = \sum_y C_y \frac{C_{xy}}{C_y}$$

$$\rightsquigarrow C_x = \mu_x.$$

Notice  $\mu_x P_{xy} = C_{xy} = C_{yx} = \mu_y P_{yx}$ , so **the chain is reversible**.

---


$$P_{xy} = C_{xy}/C_x$$

$$C_x = \mu_x$$

## Reversible chains and resistors

Let  $n_x = \mathbf{E}_a$ (number of visits to  $x$  before absorbed in  $b$ ). Then

$$n_x = \sum_y n_y P_{yx} = \sum_y \frac{C_{xy}}{C_y} n_y$$

---

$$P_{xy} = C_{xy}/C_x$$

$$C_x = \mu_x$$

## Reversible chains and resistors

Let  $n_x = \mathbf{E}_a$ (number of visits to  $x$  before absorbed in  $b$ ). Then

$$n_x = \sum_y n_y P_{yx} = \sum_y \frac{C_{xy}}{C_y} n_y$$

$$u_x = \sum_y \frac{C_{xy}}{C_x} \cdot u_y$$

## Reversible chains and resistors

Let  $n_x = \mathbf{E}_a$ (number of visits to  $x$  before absorbed in  $b$ ). Then

$$n_x = \sum_y n_y P_{yx} = \sum_y \frac{C_{xy}}{C_y} n_y$$

$$u_x = \sum_y \frac{C_{xy}}{C_x} \cdot u_y$$

$$u_x C_x = \sum_y \frac{C_{xy}}{C_y} \cdot u_y C_y$$

## Reversible chains and resistors

Let  $n_x = \mathbf{E}_a$ (number of visits to  $x$  before absorbed in  $b$ ). Then

$$n_x = \sum_y n_y P_{yx} = \sum_y \frac{C_{xy}}{C_y} n_y$$

$$u_x = \sum_y \frac{C_{xy}}{C_x} \cdot u_y$$

$$u_x C_x = \sum_y \frac{C_{xy}}{C_y} \cdot u_y C_y$$

$$\rightsquigarrow u_x C_x = n_x.$$

## Reversible chains and resistors

Let  $n_x = \mathbf{E}_a$  (number of visits to  $x$  before absorbed in  $b$ ). Then

$$n_x = \sum_y n_y P_{yx} = \sum_y \frac{C_{xy}}{C_y} n_y$$

$$u_x = \sum_y \frac{C_{xy}}{C_x} \cdot u_y$$

$$u_x C_x = \sum_y \frac{C_{xy}}{C_y} \cdot u_y C_y$$

$$\rightsquigarrow u_x C_x = n_x.$$

$\mathbf{E}_a$  (signed current  $x \rightarrow y$  before absorbed in  $b$ )

$$= n_x P_{xy} - n_y P_{yx} = (u_x - u_y) C_{xy} = i_{xy}. \quad \text{normalisation...}$$

---


$$P_{xy} = C_{xy}/C_x$$

$$C_x = \mu_x$$




# Reducing a network

Series:



$$R_{\text{eff}} = R + Q$$


Parallel:

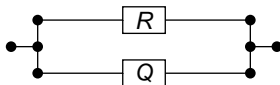

$$\frac{1}{R_{\text{eff}}} = \frac{1}{R} + \frac{1}{Q}$$

# Reducing a network

Star-Delta:

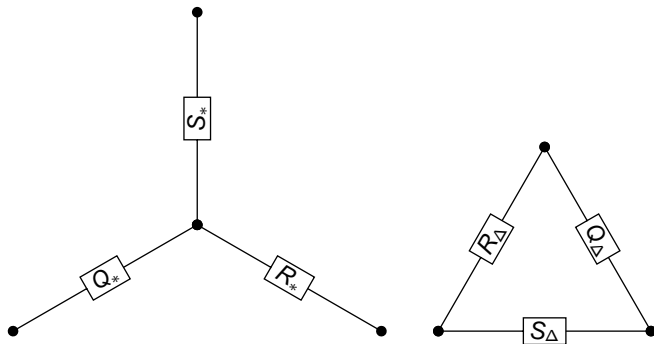


$$R_* = \frac{Q_\Delta S_\Delta}{R_\Delta + Q_\Delta + S_\Delta},$$

$$R_\Delta = \frac{R_* Q_* + R_* S_* + Q_* S_*}{R_*}.$$

# Thomson, Dirichlet principles


Thomson principle:

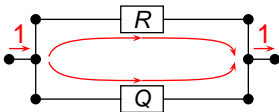

The physical unit current is the unit flow that minimizes the sum of the ohmic power losses  $\sum i^2 R$ .


# Thomson, Dirichlet principles

Thomson principle:

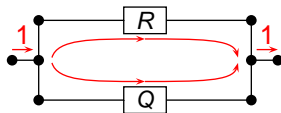

The physical unit current is the unit flow that minimizes the sum of the ohmic power losses  $\sum i^2 R$ .

Dirichlet principle:

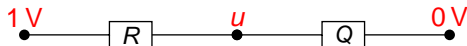

The physical voltage is the function that minimizes the ohmic power losses  $\sum (\nabla u)^2 / R$ .

# Monotonicity, transience, recurrence

## The monotonicity property:

Between any disjoint sets of vertices, the effective resistance is a non-decreasing function of the individual resistances.


# Monotonicity, transience, recurrence

## The monotonicity property:

Between any disjoint sets of vertices, the effective resistance is a non-decreasing function of the individual resistances.

↪ can be used to prove transience-recurrence by reducing the graph to something manageable in terms of resistor networks.


# The part

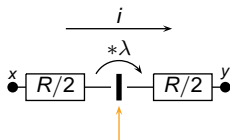

**Voltage amplifier:** keeps the current, multiplies the potential.

$$\left(u_x - i \cdot \frac{R}{2}\right) \cdot \lambda - i \cdot \frac{R}{2} = u_y$$

# The part

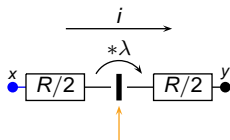


**Voltage amplifier:** keeps the current, multiplies the potential.

$$\left(u_x - i \cdot \frac{R}{2}\right) \cdot \lambda - i \cdot \frac{R}{2} = u_y$$




# The part

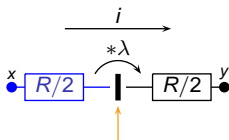

**Voltage amplifier:** keeps the current, multiplies the potential.

$$\left(u_x - i \cdot \frac{R}{2}\right) \cdot \lambda - i \cdot \frac{R}{2} = u_y$$


# The part

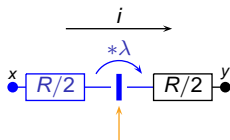

**Voltage amplifier:** keeps the current, multiplies the potential.

$$\left(u_x - i \cdot \frac{R}{2}\right) \cdot \lambda - i \cdot \frac{R}{2} = u_y$$


# The part

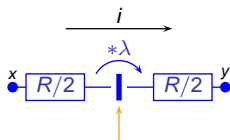

**Voltage amplifier:** keeps the current, multiplies the potential.

$$\left(u_x - i \cdot \frac{R}{2}\right) \cdot \lambda - i \cdot \frac{R}{2} = u_y$$

# The part

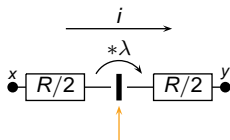

**Voltage amplifier:** keeps the current, multiplies the potential.


$$(u_x - i \cdot \frac{R}{2}) \cdot \lambda - i \cdot \frac{R}{2} = u_y$$

**Equivalent:**

$$(u_x - i \cdot R^{pr}) \cdot \lambda^{pr} = u_y$$

$$u_x \cdot \lambda^{se} - R^{se} \cdot i = u_y$$

# The part

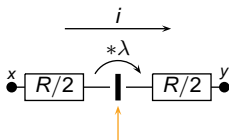

**Voltage amplifier:** keeps the current, multiplies the potential.

$$(u_x - i \cdot \frac{R}{2}) \cdot \lambda - i \cdot \frac{R}{2} = u_y$$

**Equivalent:**


$$(u_x - i \cdot R^{pr}) \cdot \lambda^{pr} = u_y$$

$$\lambda^{pr} = \lambda$$

$$u_x \cdot \lambda^{se} - R^{se} \cdot i = u_y$$

$$\lambda^{se} = \lambda$$

# The part

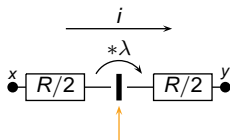

**Voltage amplifier:** keeps the current, multiplies the potential.

$$(u_x - i \cdot \frac{R}{2}) \cdot \lambda - i \cdot \frac{R}{2} = u_y$$

**Equivalent:**

$$(u_x - i \cdot R^{pr}) \cdot \lambda^{pr} = u_y$$

$$\lambda^{pr} = \lambda$$


$$R^{pr} = \frac{\lambda+1}{2\lambda} \cdot R$$

$$u_x \cdot \lambda^{se} - R^{se} \cdot i = u_y$$

$$\lambda^{se} = \lambda$$

$$R^{se} = \frac{\lambda+1}{2} \cdot R$$

# The part

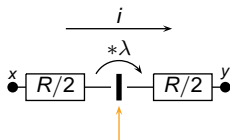

**Voltage amplifier:** keeps the current, multiplies the potential.

$$(u_x - i \cdot \frac{R}{2}) \cdot \lambda - i \cdot \frac{R}{2} = u_y$$

**Equivalent:**

$$(u_x - i \cdot R^{pr}) \cdot \lambda^{pr} = u_y$$

$$\lambda^{pr} = \lambda$$

$$R^{pr} = \frac{\lambda+1}{2\lambda} \cdot R$$

$$u_x \cdot \lambda^{se} - R^{se} \cdot i = u_y$$

$$\lambda^{se} = \lambda$$


$$R^{se} = \frac{\lambda+1}{2} \cdot R$$

---


$$R^{pr} = \frac{\lambda+1}{2\lambda} \cdot R$$

$$R^{se} = \frac{\lambda+1}{2} \cdot R$$

# Harmonicity

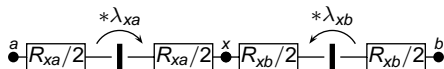


$$R^{\text{pr}} = \frac{\lambda+1}{2\lambda} \cdot R$$

$$R^{\text{se}} = \frac{\lambda+1}{2} \cdot R$$




# Harmonicity

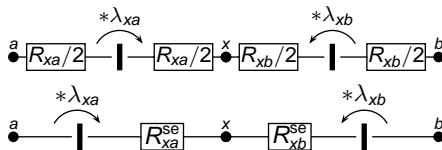

$$R^{pr} = \frac{\lambda+1}{2\lambda} \cdot R$$

$$R^{se} = \frac{\lambda+1}{2} \cdot R$$

# Harmonicity

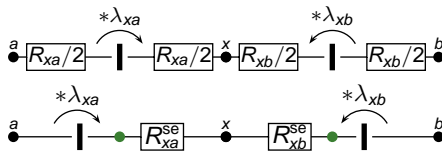


$$U_x = \sum_y \frac{C_{xy}^{se}}{\sum_z C_{xz}^{se}} \cdot \lambda_{xy} U_y$$

$$R^{pr} = \frac{\lambda+1}{2\lambda} \cdot R$$

$$R^{se} = \frac{\lambda+1}{2} \cdot R$$

# Harmonicity

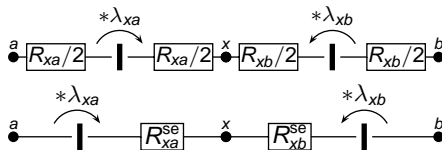


$$u_x = \sum_y \frac{C_{xy}^{se}}{\sum_z C_{xz}^{se}} \cdot \lambda_{xy} u_y$$

$$R^{pr} = \frac{\lambda+1}{2\lambda} \cdot R$$

$$R^{se} = \frac{\lambda+1}{2} \cdot R$$

# Harmonicity

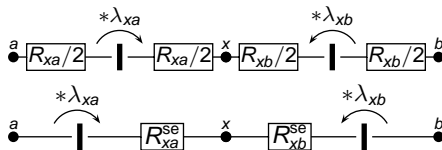


$$u_x = \sum_y \frac{C_{xy}^{se}}{\sum_z C_{xz}^{se}} \cdot \lambda_{xy} u_y = \sum_y \frac{C_{xy} \frac{2}{\lambda_{xy} + 1}}{\sum_z C_{xz} \frac{2}{\lambda_{xz} + 1}} \cdot \lambda_{xy} u_y$$

$$R^{pr} = \frac{\lambda + 1}{2\lambda} \cdot R$$

$$R^{se} = \frac{\lambda + 1}{2} \cdot R$$

# Harmonicity

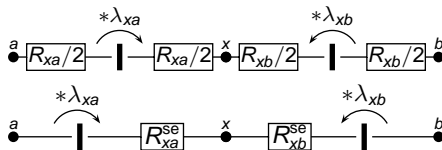


$$u_x = \sum_y \frac{C_{xy}^{se}}{\sum_z C_{xz}^{se}} \cdot \lambda_{xy} u_y = \sum_y \frac{C_{xy} \frac{2}{\lambda_{xy} + 1}}{\sum_z C_{xz} \frac{2}{\lambda_{xz} + 1}} \cdot \lambda_{xy} u_y$$

$$R^{pr} = \frac{\lambda + 1}{2\lambda} \cdot R$$

$$R^{se} = \frac{\lambda + 1}{2} \cdot R$$

# Harmonicity

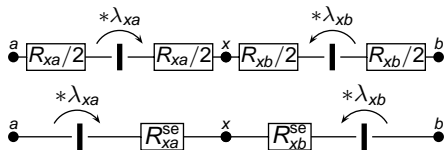


$$\begin{aligned}
 u_x &= \sum_y \frac{C_{xy}^{se}}{\sum_z C_{xz}^{se}} \cdot \lambda_{xy} u_y = \sum_y \frac{C_{xy} \frac{2}{\lambda_{xy} + 1}}{\sum_z C_{xz} \frac{2}{\lambda_{xz} + 1}} \cdot \lambda_{xy} u_y \\
 &= \sum_y \frac{D_{xy} \gamma_{xy}}{\sum_z D_{xz} \gamma_{zx}} \cdot u_y
 \end{aligned}$$

with  $\gamma_{xy} = \sqrt{\lambda_{xy}} = 1/\gamma_{yx}$ ,  $D_{xy} = 2\gamma_{xy} C_{xy}/(\lambda_{xy} + 1) = D_{yx}$ .

$$R^{pr} = \frac{\lambda+1}{2\lambda} \cdot R$$

$$R^{se} = \frac{\lambda+1}{2} \cdot R$$

# Harmonicity

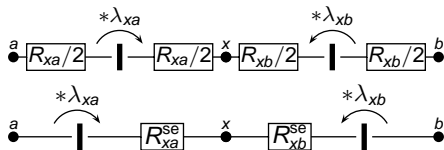


$$\begin{aligned}
 u_x &= \sum_y \frac{C_{xy}^{se}}{\sum_z C_{xz}^{se}} \cdot \lambda_{xy} u_y = \sum_y \frac{C_{xy} \frac{2}{\lambda_{xy} + 1}}{\sum_z C_{xz} \frac{2}{\lambda_{xz} + 1}} \cdot \lambda_{xy} u_y \\
 &= \sum_y \frac{D_{xy} \gamma_{xy}}{\sum_z D_{xz} \gamma_{zx}} \cdot u_y
 \end{aligned}$$

with  $\gamma_{xy} = \sqrt{\lambda_{xy}} = 1/\gamma_{yx}$ ,  $D_{xy} = 2\gamma_{xy} C_{xy}/(\lambda_{xy} + 1) = D_{yx}$ .

$$R^{pr} = \frac{\lambda+1}{2\lambda} \cdot R$$

$$R^{se} = \frac{\lambda+1}{2} \cdot R$$

# Harmonicity

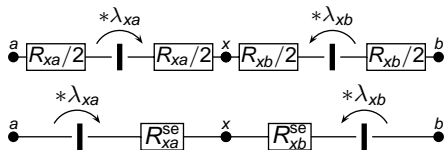

$$\begin{aligned}
 u_x &= \sum_y \frac{C_{xy}^{se}}{\sum_z C_{xz}^{se}} \cdot \lambda_{xy} u_y = \sum_y \frac{C_{xy} \frac{2}{\lambda_{xy} + 1}}{\sum_z C_{xz} \frac{2}{\lambda_{xz} + 1}} \cdot \lambda_{xy} u_y \\
 &= \sum_y \frac{D_{xy} \gamma_{xy}}{\sum_z D_{xz} \gamma_{zx}} \cdot u_y = \sum_y \frac{D_{xy} \gamma_{xy}}{D_x} \cdot u_y
 \end{aligned}$$


with  $\gamma_{xy} = \sqrt{\lambda_{xy}} = 1/\gamma_{yx}$ ,  $D_{xy} = 2\gamma_{xy} C_{xy}/(\lambda_{xy} + 1) = D_{yx}$ .

$$R^{pr} = \frac{\lambda+1}{2\lambda} \cdot R$$

$$R^{se} = \frac{\lambda+1}{2} \cdot R$$



# Harmonicity

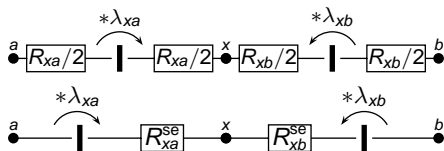

$$\begin{aligned}
 u_x &= \sum_y \frac{C_{xy}^{se}}{\sum_z C_{xz}^{se}} \cdot \lambda_{xy} u_y = \sum_y \frac{C_{xy} \frac{2}{\lambda_{xy} + 1}}{\sum_z C_{xz} \frac{2}{\lambda_{xz} + 1}} \cdot \lambda_{xy} u_y \\
 &= \sum_y \frac{D_{xy} \gamma_{xy}}{\sum_z D_{xz} \gamma_{zx}} \cdot u_y = \sum_y \frac{D_{xy} \gamma_{xy}}{D_x} \cdot u_y
 \end{aligned}$$

with  $\gamma_{xy} = \sqrt{\lambda_{xy}} = 1/\gamma_{yx}$ ,  $D_{xy} = 2\gamma_{xy} C_{xy}/(\lambda_{xy} + 1) = D_{yx}$ .

---


$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} \quad D_{xy} = 2\gamma_{xy} C_{xy}/(\lambda_{xy} + 1)$$

## From network to chain

**Irreducible Markov chain:** on  $\Omega$ ,  $a \neq b$ ,  $x \in \Omega$ ,

$$h_x := \mathbf{P}_x\{\tau_a < \tau_b\} \quad (\tau \text{ is the hitting time})$$

is **harmonic**:

$$h_x = \sum_y P_{xy} h_y, \quad h_a = 1, \quad h_b = 0.$$

$$u_x = \sum_y \frac{D_{xy} \gamma_{xy}}{D_x} \cdot u_y, \quad u_a = 1, \quad u_b = 0.$$

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} \quad D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

## From network to chain

**Irreducible Markov chain:** on  $\Omega$ ,  $a \neq b$ ,  $x \in \Omega$ ,

$$h_x := \mathbf{P}_x\{\tau_a < \tau_b\} \quad (\tau \text{ is the hitting time})$$

is **harmonic**:

$$h_x = \sum_y P_{xy} h_y, \quad h_a = 1, \quad h_b = 0.$$

$$u_x = \sum_y \frac{D_{xy} \gamma_{xy}}{D_x} \cdot u_y, \quad u_a = 1, \quad u_b = 0.$$

$$P_{xy} = \frac{D_{xy} \gamma_{xy}}{D_x}.$$

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} \quad D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

## From network to chain

**Irreducible Markov chain:** on  $\Omega$ ,  $a \neq b$ ,  $x \in \Omega$ ,

$$h_x := \mathbf{P}_x\{\tau_a < \tau_b\} \quad (\tau \text{ is the hitting time})$$

is **harmonic**:

$$h_x = \sum_y P_{xy} h_y, \quad h_a = 1, \quad h_b = 0.$$

$$u_x = \sum_y \frac{D_{xy} \gamma_{xy}}{D_x} \cdot u_y, \quad u_a = 1, \quad u_b = 0.$$

$$P_{xy} = \frac{D_{xy} \gamma_{xy}}{D_x}.$$

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} \quad D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$

# From network to chain

Stationary distribtuion:

$$\mu_x = \sum_z \mu_z P_{zx} = \sum_z \mu_z \frac{D_{zx} \gamma_{zx}}{D_z}$$

$$D_x = \sum_z D_z \frac{D_{zx} \gamma_{zx}}{D_z}$$

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} \quad D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$

# From network to chain

Stationary distribtuion:

$$\mu_x = \sum_z \mu_z P_{zx} = \sum_z \mu_z \frac{D_{zx} \gamma_{zx}}{D_z}$$

$$D_x = \sum_z D_z \frac{D_{zx} \gamma_{zx}}{D_z}$$

$$\rightsquigarrow D_x = \mu_x.$$

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} \quad D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$

## "Markovity" property

$$u_x = \sum_z P_{xz} u_z; \quad \sum_z P_{xz} = 1$$

$u_x \equiv \text{const.}$  is a solution of the network with no external sources. This is now nontrivial.

---


$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx}$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$

$$D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

## "Markovity" property

$$u_x = \sum_z P_{xz} u_z; \quad \sum_z P_{xz} = 1$$

$u_x \equiv \text{const.}$  is a solution of the network with no external sources. This is now nontrivial.

$$\sum_z P_{xz} = \sum_z \frac{D_{xz} \gamma_{xz}}{D_x} = 1$$

$$D_x := \sum_z D_{xz} \gamma_{zx}$$

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx}$$

$$D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$



# "Markovity" property

$$u_x = \sum_z P_{xz} u_z; \quad \sum_z P_{xz} = 1$$

$u_x \equiv \text{const.}$  is a solution of the network with no external sources. This is now nontrivial.

$$\sum_z P_{xz} = \sum_z \frac{D_{xz} \gamma_{xz}}{D_x} = 1$$

$$D_x := \sum_z D_{xz} \gamma_{zx} = \sum_z D_{xz} \gamma_{xz}.$$

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx}$$

$$D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$

## "Markovity" property

$$u_x = \sum_z P_{xz} u_z; \quad \sum_z P_{xz} = 1$$

$u_x \equiv \text{const.}$  is a solution of the network with no external sources. This is now nontrivial.

$$\sum_z P_{xz} = \sum_z \frac{D_{xz} \gamma_{xz}}{D_x} = 1$$

$$D_x := \sum_z D_{xz} \gamma_{zx} = \sum_z D_{xz} \gamma_{xz}.$$

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} = \sum_z D_{xz} \gamma_{xz} \quad D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$

# From chain to network

$$P_{xy} = \frac{D_{xy}\gamma_{xy}}{D_x} = \frac{D_{xy}\gamma_{xy}}{\mu_x}$$

$$\mu_x P_{xy} \cdot \mu_y P_{yx} = D_{xy}^2;$$

$$\frac{\mu_x P_{xy}}{\mu_y P_{yx}} = \gamma_{xy}^2 = \lambda_{xy}.$$

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz}\gamma_{zx} = \sum_z D_{xz}\gamma_{xz} \quad D_{xy} = 2\gamma_{xy}C_{xy}/(\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy}\gamma_{xy}/D_x$$

## From chain to network

$$P_{xy} = \frac{D_{xy}\gamma_{xy}}{D_x} = \frac{D_{xy}\gamma_{xy}}{\mu_x}$$

$$\mu_x P_{xy} \cdot \mu_y P_{yx} = D_{xy}^2;$$

$$\frac{\mu_x P_{xy}}{\mu_y P_{yx}} = \gamma_{xy}^2 = \lambda_{xy}.$$

**Reversed chain:** Replace  $P_{xy}$  by  $\hat{P}_{xy} = P_{yx} \cdot \frac{\mu_y}{\mu_x}$ .

$\rightsquigarrow$   $D_{xy}$  stays,  $\lambda_{xy}$  reverses to  $\lambda_{yx}$ .

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz}\gamma_{zx} = \sum_z D_{xz}\gamma_{xz} \quad D_{xy} = 2\gamma_{xy}C_{xy}/(\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy}\gamma_{xy}/D_x$$

## From chain to network

Let  $n_x = \mathbf{E}_a$ (number of visits to  $x$  before absorbed in  $b$ ). Then

$$n_x = \sum_y n_y P_{yx} = \sum_y \frac{D_{yx} \gamma_{yx}}{D_y} n_y$$

---


$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} = \sum_z D_{xz} \gamma_{xz} \quad D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$

## From chain to network

Let  $n_x = \mathbf{E}_a$  (number of visits to  $x$  before absorbed in  $b$ ). Then

$$n_x = \sum_y n_y P_{yx} = \sum_y \frac{D_{yx} \gamma_{yx}}{D_y} n_y$$

$$u_x = \sum_y \frac{D_{xy} \gamma_{xy}}{D_x} \cdot u_y$$

---


$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} = \sum_z D_{xz} \gamma_{xz} \quad D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$

## From chain to network

Let  $n_x = \mathbf{E}_a$  (number of visits to  $x$  before absorbed in  $b$ ). Then

$$n_x = \sum_y n_y P_{yx} = \sum_y \frac{D_{yx} \gamma_{yx}}{D_y} n_y$$

$$u_x = \sum_y \frac{D_{xy} \gamma_{xy}}{D_x} \cdot u_y$$

$$u_x D_x = \sum_y \frac{D_{xy} \gamma_{xy}}{D_y} \cdot u_y D_y$$

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} = \sum_z D_{xz} \gamma_{xz} \quad D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$

## From chain to network

Let  $n_x = \mathbf{E}_a$  (number of visits to  $x$  before absorbed in  $b$ ). Then

$$n_x = \sum_y n_y P_{yx} = \sum_y \frac{D_{yx} \gamma_{yx}}{D_y} n_y$$

$$u_x = \sum_y \frac{D_{xy} \gamma_{xy}}{D_x} \cdot u_y$$

$$u_x D_x = \sum_y \frac{D_{xy} \gamma_{xy}}{D_y} \cdot u_y D_y$$

$$\rightsquigarrow \hat{u}_x D_x = n_x$$

in the reversed chain.

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} = \sum_z D_{xz} \gamma_{xz} \quad D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$



## From chain to network

Let  $n_x = \mathbf{E}_a$ (number of visits to  $x$  before absorbed in  $b$ ). Then

$$\rightsquigarrow \hat{u}_x D_x = n_x$$

in the reversed chain.

$\mathbf{E}_a$ (signed current  $x \rightarrow y$  before absorbed in  $b$ )

$$= n_x P_{xy} - n_y P_{yx} = (\hat{u}_x \gamma_{xy} - \hat{u}_y \gamma_{yx}) D_{xy} = \hat{i}_{xy}. \quad \text{normalisation...}$$

$$\gamma_{xy} = \sqrt{\lambda_{xy}} \quad D_x = \sum_z D_{xz} \gamma_{zx} = \sum_z D_{xz} \gamma_{xz} \quad D_{xy} = 2\gamma_{xy} C_{xy} / (\lambda_{xy} + 1)$$

$$P_{xy} = D_{xy} \gamma_{xy} / D_x$$

## Effective resistance

Suppose  $u_a, u_b$  given, the solution is  $\{u_x\}_{x \in \Omega}$  and  $\{i_{xy}\}_{x \sim y \in \Omega}$ .

Current

$$i_a = \sum_{x \sim a} i_{ax}$$

flows in the network at  $a$ .

## Effective resistance

Suppose  $u_a, u_b$  given, the solution is  $\{u_x\}_{x \in \Omega}$  and  $\{i_{xy}\}_{x \sim y \in \Omega}$ .

Current

$$i_a = \sum_{x \sim a} i_{ax}$$

flows in the network at  $a$ .

$\rightsquigarrow$  **The "Markovity" property** has another solution: constant  $u_b$  potentials with zero external currents.

## Effective resistance

Suppose  $u_a, u_b$  given, the solution is  $\{u_x\}_{x \in \Omega}$  and  $\{i_{xy}\}_{x \sim y \in \Omega}$ .

Current

$$i_a = \sum_{x \sim a} i_{ax}$$

flows in the network at  $a$ .

↪ **The "Markovity" property** has another solution: constant  $u_b$  potentials with zero external currents.

↪ The difference of these two:  $\{u_x - u_b\}_{x \in \Omega}$  is a solution too, with  $i_a$  flowing in the network.

## Effective resistance

Suppose  $u_a, u_b$  given, the solution is  $\{u_x\}_{x \in \Omega}$  and  $\{i_{xy}\}_{x \sim y \in \Omega}$ .

Current

$$i_a = \sum_{x \sim a} i_{ax}$$

flows in the network at  $a$ .

↪ **The "Markovity" property** has another solution: constant  $u_b$  potentials with zero external currents.

↪ The difference of these two:  $\{u_x - u_b\}_{x \in \Omega}$  is a solution too, with  $i_a$  flowing in the network.

↪ Going backwards from  $u_b - u_b = 0$  at  $b$ , all currents and potentials are proportional to  $u_a - u_b$  at  $a$ .

## Effective resistance

Suppose  $u_a, u_b$  given, the solution is  $\{u_x\}_{x \in \Omega}$  and  $\{i_{xy}\}_{x \sim y \in \Omega}$ .

Current

$$i_a = \sum_{x \sim a} i_{ax}$$

flows in the network at  $a$ .

↪ **The "Markovity" property** has another solution: constant  $u_b$  potentials with zero external currents.

↪ The difference of these two:  $\{u_x - u_b\}_{x \in \Omega}$  is a solution too, with  $i_a$  flowing in the network.

↪ Going backwards from  $u_b - u_b = 0$  at  $b$ , all currents and potentials are proportional to  $u_a - u_b$  at  $a$ .

↪ In particular,  $i_a$  is proportional to  $u_a - u_b$ . **We have effective resistance.**

# What works

... the analogy with  $\mathbf{P}\{\tau_a < \tau_b\}$ .

# What works

... the analogy with  $\mathbf{P}\{\tau_a < \tau_b\}$ .

Modulo normalisation...

$$\mathbf{E}_a(\text{signed current } x \rightarrow y \text{ before absorbed in } b) = \hat{i}_{xy}.$$

in the reversed network!



# What works

... the analogy with  $\mathbf{P}\{\tau_a < \tau_b\}$ .

Modulo normalisation...

$$\mathbf{E}_a(\text{signed current } x \rightarrow y \text{ before absorbed in } b) = \hat{i}_{xy}.$$


in the reversed network!

## Theorem

*Commute time =  $R_{\text{eff}}$  · all conductances.*

# The electric network


Series:

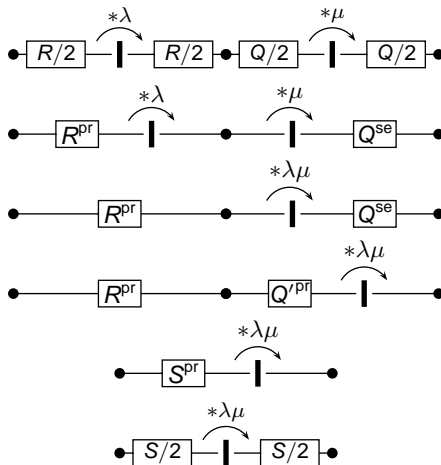


$$S = R \frac{(\lambda + 1)\mu}{\lambda\mu + 1} + Q \frac{\mu + 1}{\lambda\mu + 1}.$$

# The electric network

Parallel:

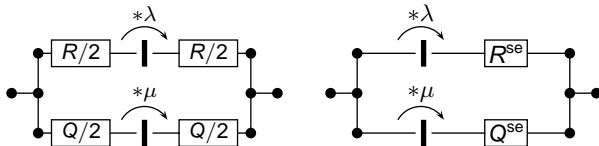

Compare this with

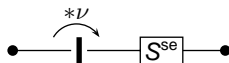

$$S = \frac{RQ}{R + Q}$$


$$\nu = \frac{Q\lambda(\mu + 1) + R\mu(\lambda + 1)}{Q(\mu + 1) + R(\lambda + 1)}$$

# The electric network

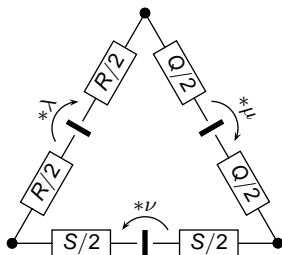
## Star-Delta:

Star to Delta works,


Delta to Star only works if Delta does not produce a circular current by itself ( $\lambda\mu\nu = 1$ ).



# Nonmonotonicity

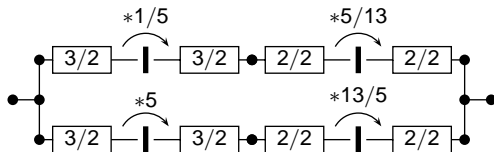

$$R_{\text{eff}} = \frac{27}{14}$$

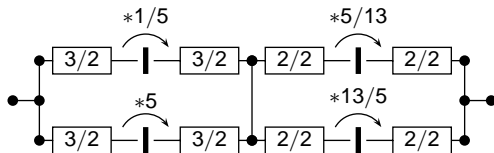

$$R_{\text{eff}} = \frac{5}{2} = \frac{35}{14}$$

# Dirichlet principle

Classical case:

# Dirichlet principle

Classical case:

$$(i_u)_{xy} = C_{xy} \cdot (u(x) - u(y)),$$
$$E_{\text{Ohm}}(i_u) = \sum_{x \sim y} (i_u)_{xy}^2 \cdot R_{xy}.$$

# Dirichlet principle

Classical case:

$$C_{\text{eff}} = E_{\text{Ohm}}(i_u),$$

$$(i_u)_{xy} = C_{xy} \cdot (u(x) - u(y)),$$

$$E_{\text{Ohm}}(i_u) = \sum_{x \sim y} (i_u)_{xy}^2 \cdot R_{xy}.$$



# Dirichlet principle

Classical case:

$$C_{\text{eff}} = \min_{u: u(a)=1, u(b)=0} E_{\text{Ohm}}(i_u),$$

$$(i_u)_{xy} = C_{xy} \cdot (u(x) - u(y)),$$

$$E_{\text{Ohm}}(i_u) = \sum_{x \sim y} (i_u)_{xy}^2 \cdot R_{xy}.$$

# Dirichlet principle

Classical case:

$$C_{\text{eff}} = \min_{u: u(a)=1, u(b)=0} E_{\text{Ohm}}(i_u),$$

$$(i_u)_{xy} = C_{xy} \cdot (u(x) - u(y)),$$

$$E_{\text{Ohm}}(i_u) = \sum_{x \sim y} (i_u)_{xy}^2 \cdot R_{xy}.$$

Irreversible case (A. Gaudillière, C. Landim / M. Slowik):

$$(i_u^*)_{xy} = \frac{2\lambda_{xy}}{\lambda_{xy} + 1} C_{xy} u(x) - \frac{2}{\lambda_{xy} + 1} C_{xy} u(y),$$

$$E_{\text{Ohm}}(i_u^* - \Psi) = \sum_{x \sim y} (i_u^* - \Psi)_{xy}^2 \cdot R_{xy}.$$

# Dirichlet principle

Classical case:

$$C_{\text{eff}} = \min_{u: u(a)=1, u(b)=0} E_{\text{Ohm}}(i_u),$$

$$(i_u)_{xy} = C_{xy} \cdot (u(x) - u(y)),$$

$$E_{\text{Ohm}}(i_u) = \sum_{x \sim y} (i_u)_{xy}^2 \cdot R_{xy}.$$

Irreversible case (A. Gaudillière, C. Landim / M. Slowik):

$$C_{\text{eff}} = E_{\text{Ohm}}(i_u^* - \Psi),$$

$$(i_u^*)_{xy} = \frac{2\lambda_{xy}}{\lambda_{xy} + 1} C_{xy} u(x) - \frac{2}{\lambda_{xy} + 1} C_{xy} u(y),$$

$$E_{\text{Ohm}}(i_u^* - \Psi) = \sum_{x \sim y} (i_u^* - \Psi)_{xy}^2 \cdot R_{xy}.$$

# Dirichlet principle

Classical case:

$$C_{\text{eff}} = \min_{u: u(a)=1, u(b)=0} E_{\text{Ohm}}(i_u),$$

$$(i_u)_{xy} = C_{xy} \cdot (u(x) - u(y)),$$

$$E_{\text{Ohm}}(i_u) = \sum_{x \sim y} (i_u)_{xy}^2 \cdot R_{xy}.$$

Irreversible case (A. Gaudillière, C. Landim / M. Slowik):

$$C_{\text{eff}} = \min_{\Psi: \text{flow}} E_{\text{Ohm}}(i_u^* - \Psi),$$

$$(i_u^*)_{xy} = \frac{2\lambda_{xy}}{\lambda_{xy} + 1} C_{xy} u(x) - \frac{2}{\lambda_{xy} + 1} C_{xy} u(y),$$

$$E_{\text{Ohm}}(i_u^* - \Psi) = \sum_{x \sim y} (i_u^* - \Psi)_{xy}^2 \cdot R_{xy}.$$

# Dirichlet principle

Classical case:

$$C_{\text{eff}} = \min_{u: u(a)=1, u(b)=0} E_{\text{Ohm}}(i_u),$$

$$(i_u)_{xy} = C_{xy} \cdot (u(x) - u(y)),$$

$$E_{\text{Ohm}}(i_u) = \sum_{x \sim y} (i_u)_{xy}^2 \cdot R_{xy}.$$

Irreversible case (A. Gaudillière, C. Landim / M. Slowik):

$$C_{\text{eff}} = \min_{u: u(a)=1, u(b)=0} \min_{\Psi: \text{flow}} E_{\text{Ohm}}(i_u^* - \Psi),$$

$$(i_u^*)_{xy} = \frac{2\lambda_{xy}}{\lambda_{xy} + 1} C_{xy} u(x) - \frac{2}{\lambda_{xy} + 1} C_{xy} u(y),$$

$$E_{\text{Ohm}}(i_u^* - \Psi) = \sum_{x \sim y} (i_u^* - \Psi)_{xy}^2 \cdot R_{xy}.$$

# Dirichlet principle

Classical case:

$$C_{\text{eff}} = \min_{u: u(a)=1, u(b)=0} E_{\text{Ohm}}(i_u),$$

$$(i_u)_{xy} = C_{xy} \cdot (u(x) - u(y)),$$

$$E_{\text{Ohm}}(i_u) = \sum_{x \sim y} (i_u)_{xy}^2 \cdot R_{xy}.$$

Irreversible case (A. Gaudillière, C. Landim / M. Slowik):

$$C_{\text{eff}} = \min_{u: u(a)=1, u(b)=0} \min_{\Psi: \text{flow}} E_{\text{Ohm}}(i_u^* - \Psi),$$

$$(i_u^*)_{xy} = \frac{2\lambda_{xy}}{\lambda_{xy} + 1} C_{xy} u(x) - \frac{2}{\lambda_{xy} + 1} C_{xy} u(y),$$

$$E_{\text{Ohm}}(i_u^* - \Psi) = \sum_{x \sim y} (i_u^* - \Psi)_{xy}^2 \cdot R_{xy}.$$

Thank you.